

ELD Assignment Booth Multiplier Group08

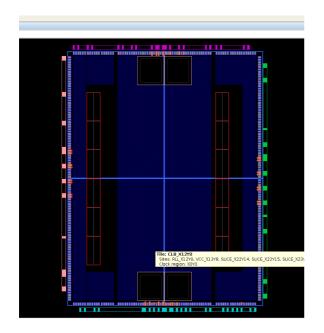
- 1. How many dedicated multipliers does the FPGA have ?
 There are 12 dedicated multipliers in Spartan 3E-250 CP132..
- 2. Where are they located physically?


 They are located along with the RAM Blocks in FPGA.
- 3. Which one does your design use?



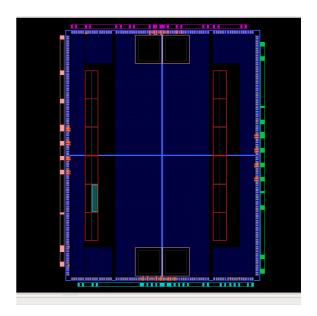

DESIGN SUMARRIES:

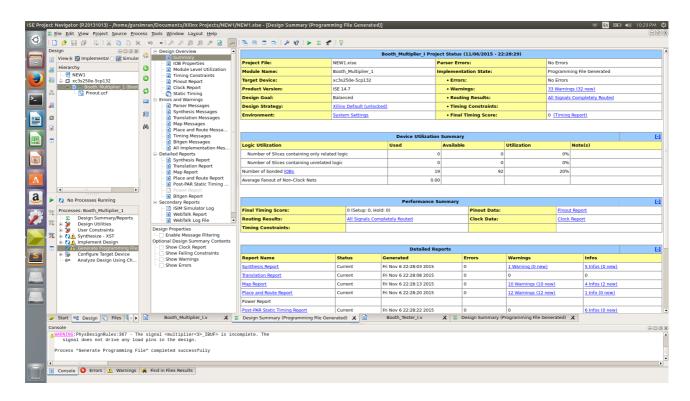

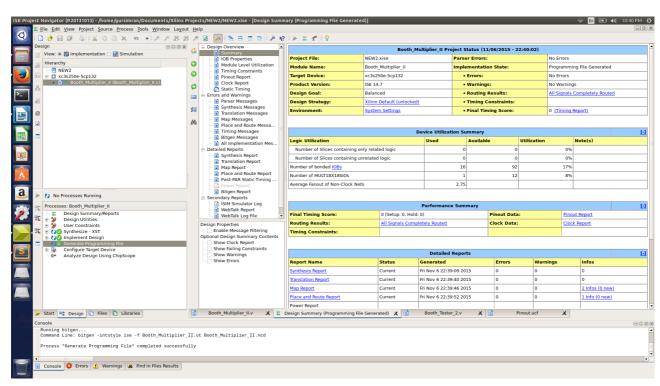

SIMULATIONS:

